

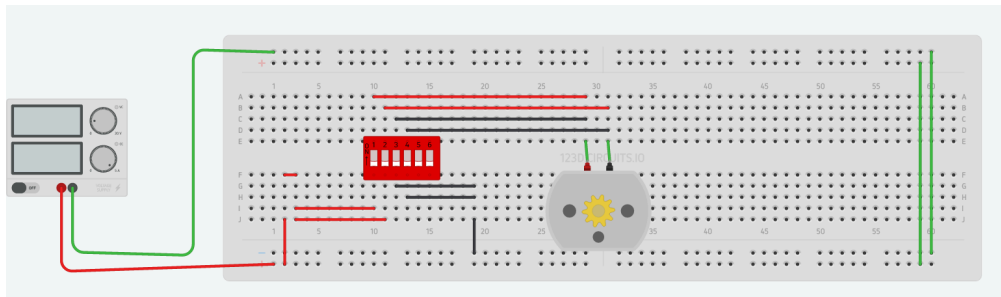



## H Bridge Part 1 – FOUR SWITCH CIRCUIT

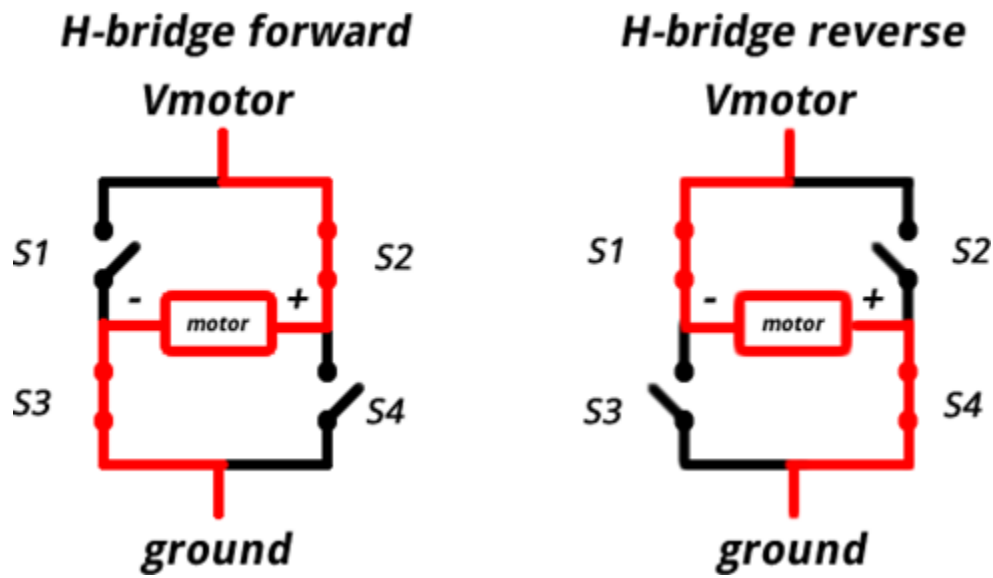

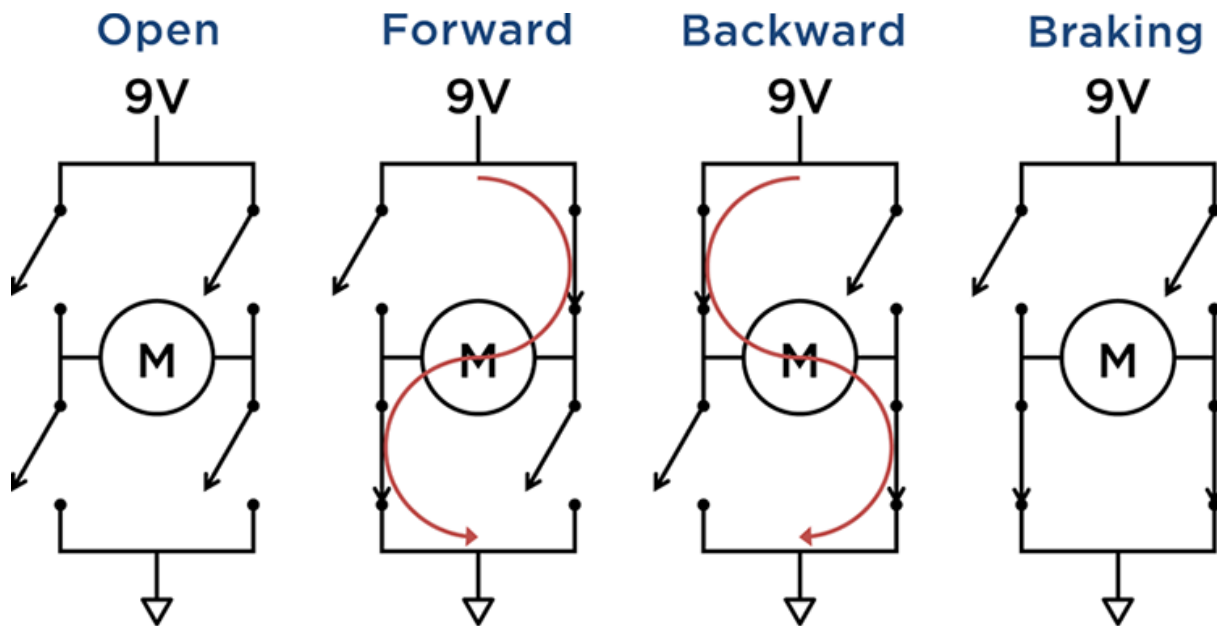


Now try creating a partial H-Bridge with Transistors

**TINKERCAD VERSION (ONLY) BELOW**

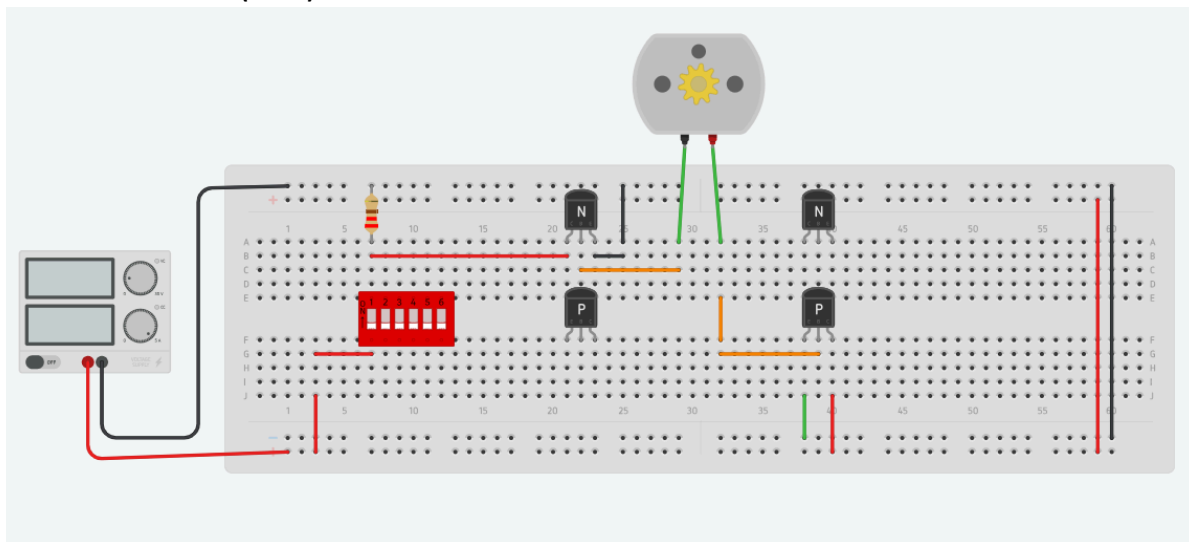

The above diagram is based on **C**BE Transistor layout pins NOT the **B**C**E** layout as your transistors

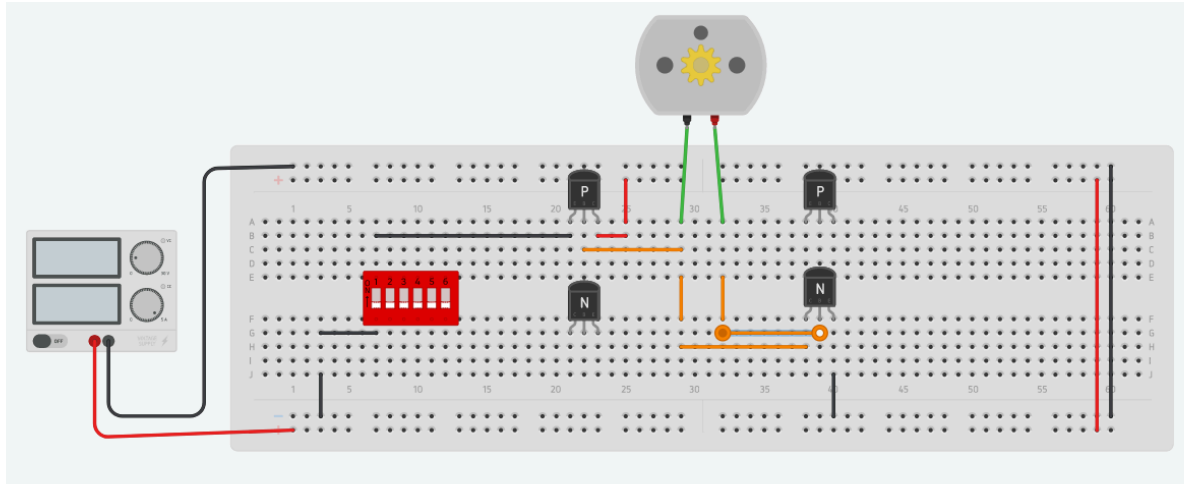IN – CLASS (ACTUAL) BREADBOARD VERSION BELOW




Notice the relation between the PNP and the NPN transistor

Follow the Positive from Power source into the Emitter on the PNP (P) transistor. Remember the N in the middle indicates a negative Base (trigger) or drain towards ground.


Positive voltage follows out of the collector.

Positive voltage goes into the motor and out and goes into the collector side of another transistor NPN (N).

Positive voltage is split coming out of the previous PNP transistor and also goes into the Base (trigger) of the NPN which indicates a positive Base (trigger) to allow voltage to flow through

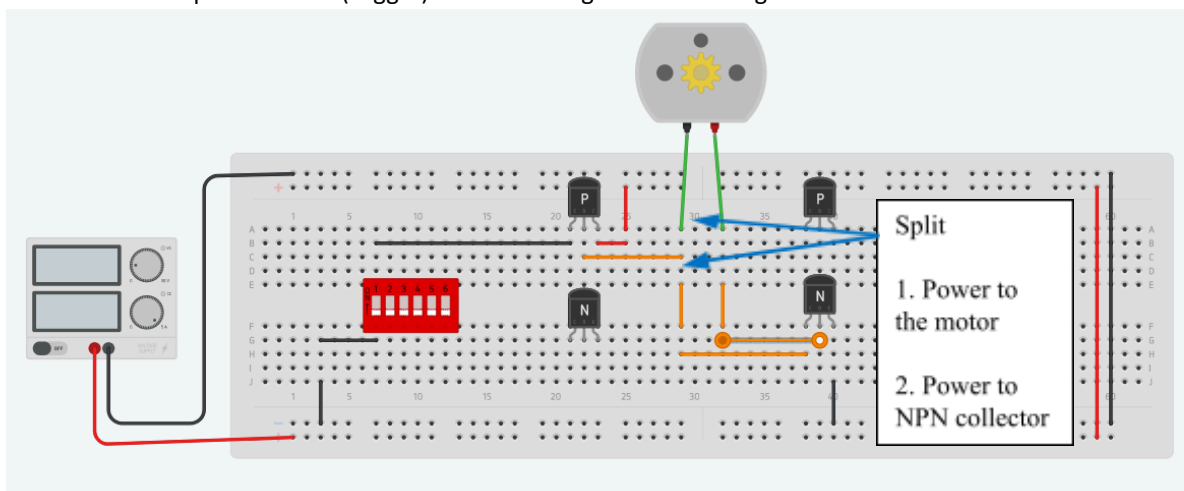


TIP 125

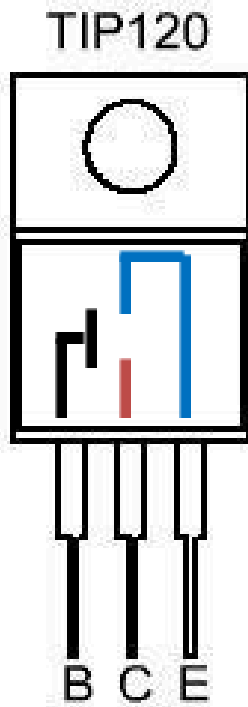

B - BASE  
C - COLLECTOR  
E - EMITTER





**NPN**


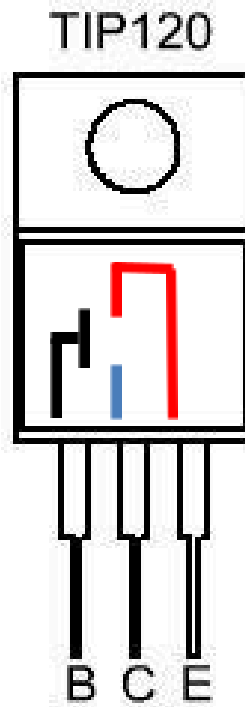


B - BASE  
C - COLLECTOR  
E - EMITTER

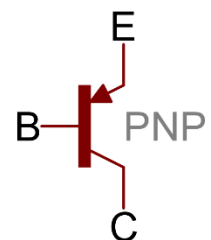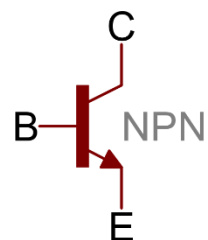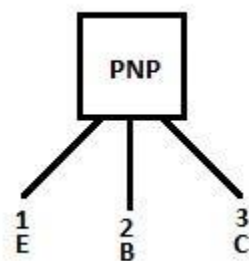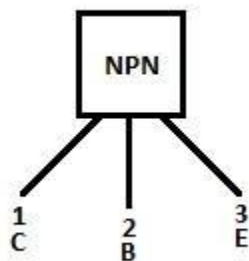**PNP**

A traditional transistor would alternately look like below (CBE OR EBC)




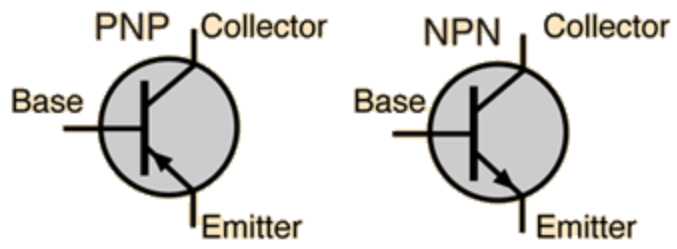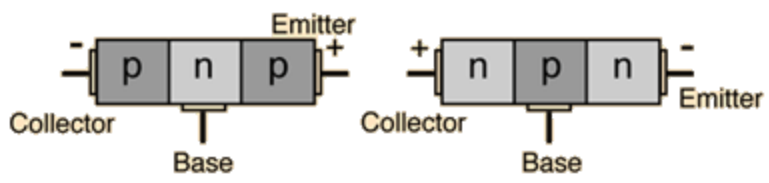

## H Bridge Full Circuit


Two different orientations.

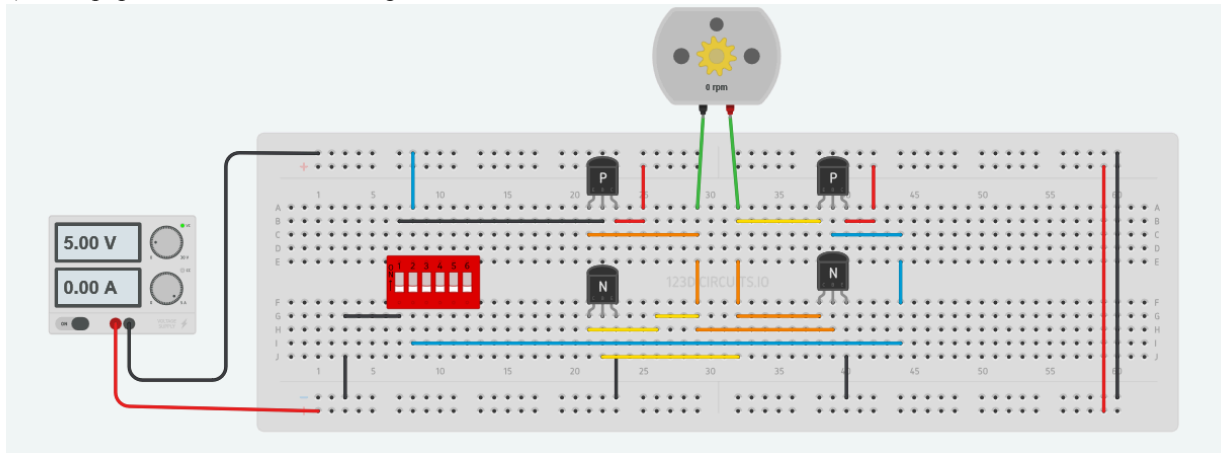1) Most popular is the PNP to the top or motor side.






Note however, the switch is connected to ground (GND) or Negative - since PNP TIP 125 base requires LOW or GND as the trigger for the BASE.

2) NPN to the top or motor side

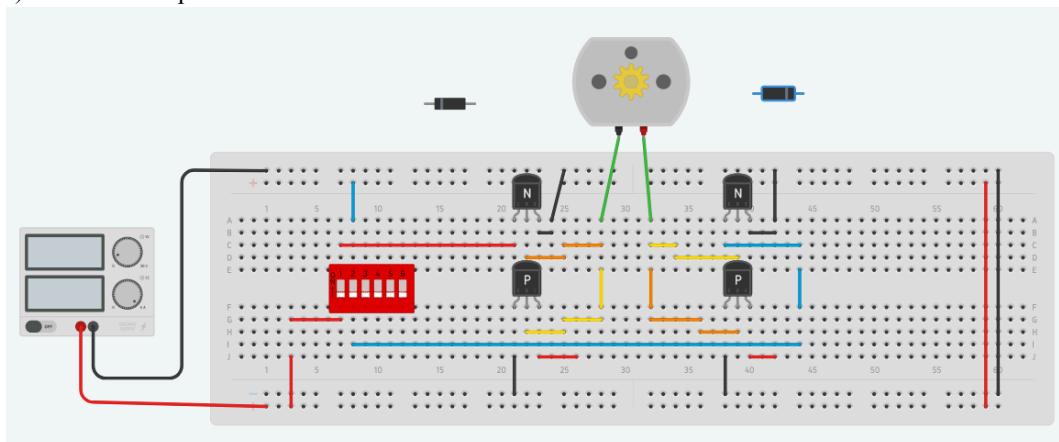


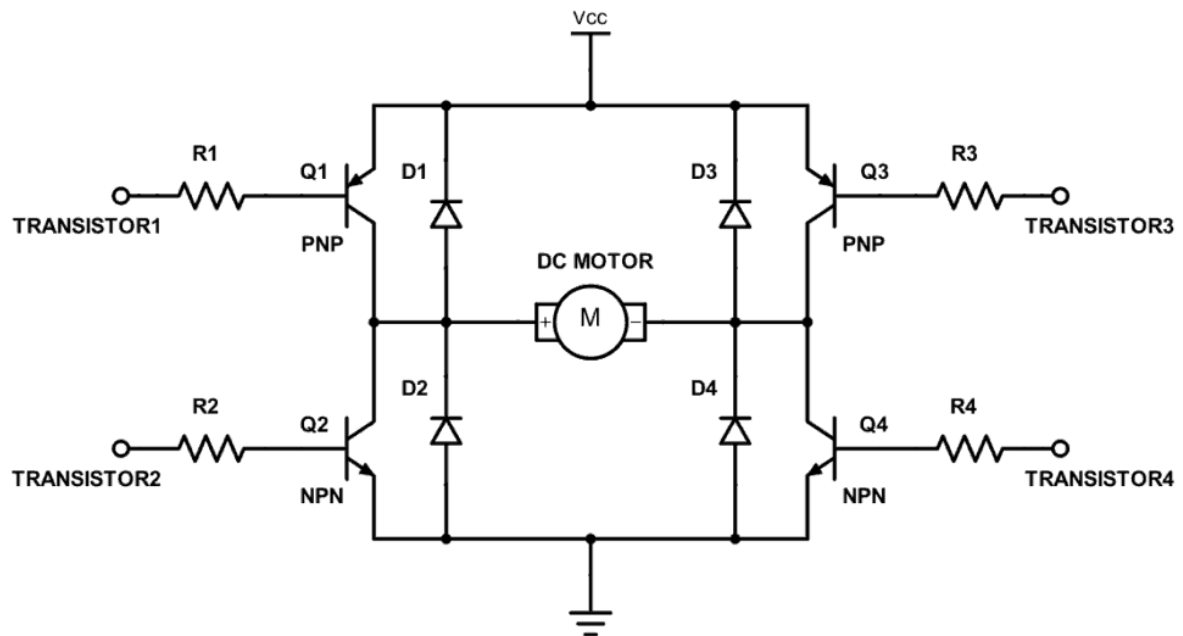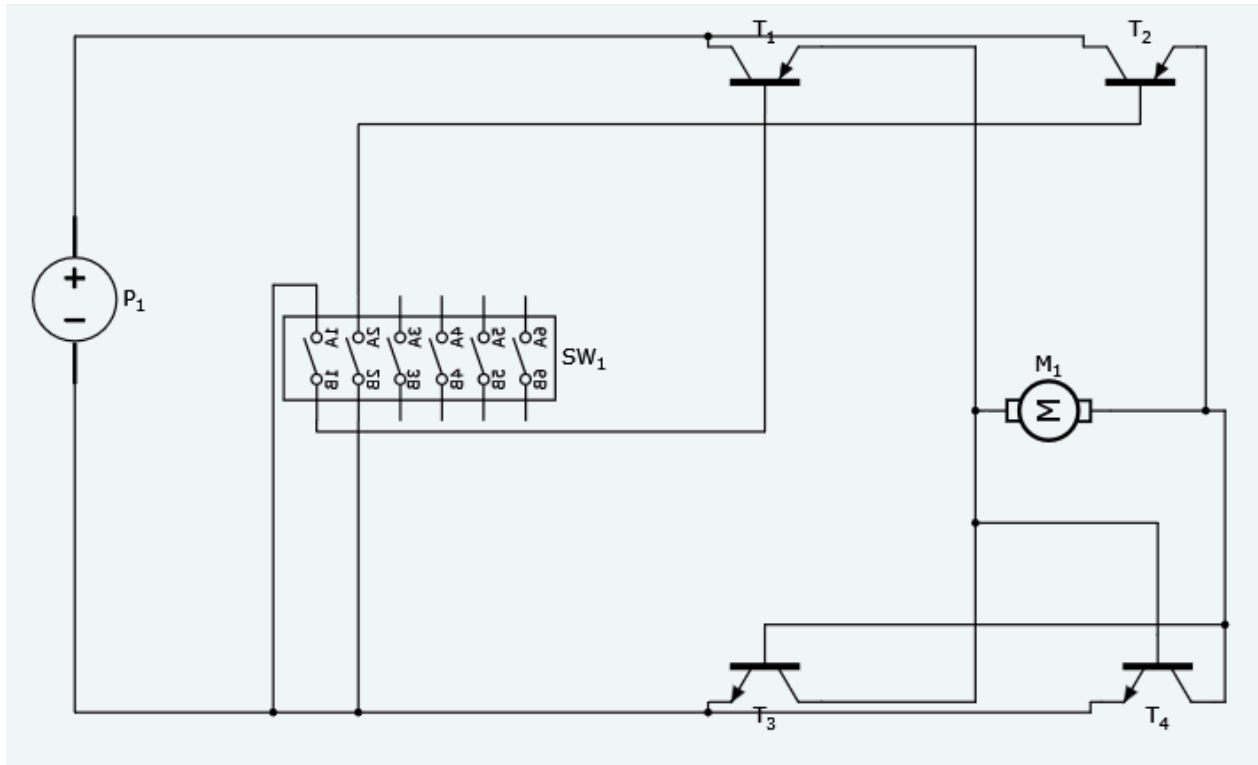Easier orientation to power as it follows a tradition power (positive current) in through the Switch (Positive - to NPN TIP 120 since the base is triggered by a positive voltage.



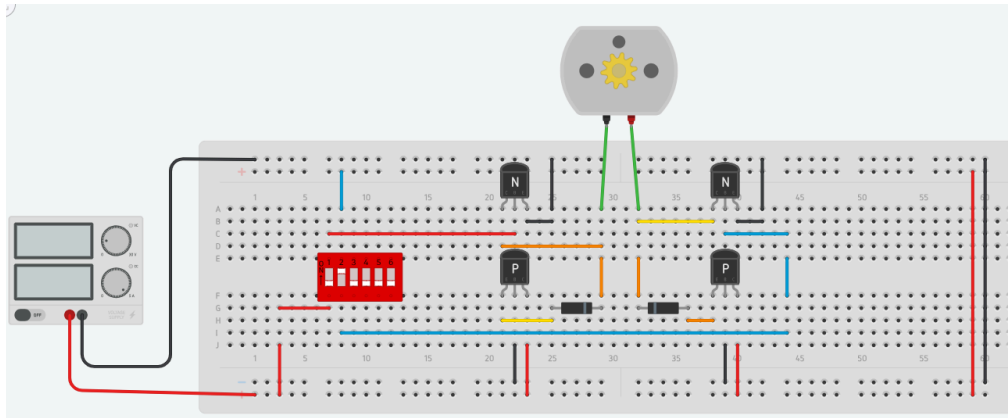

Full H Bridge with 2 Diodes

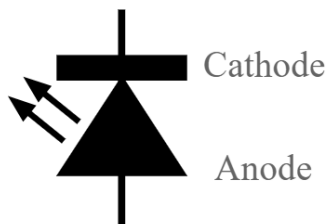


Notice LED – Light Emitting Diode has emitting arrows...






... and a standard diode does not



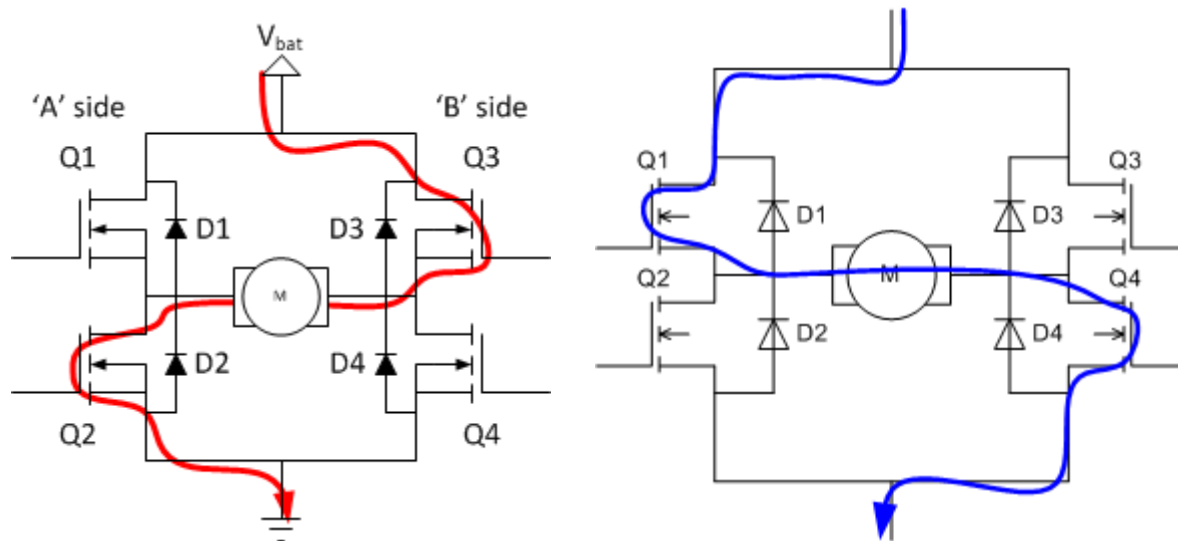

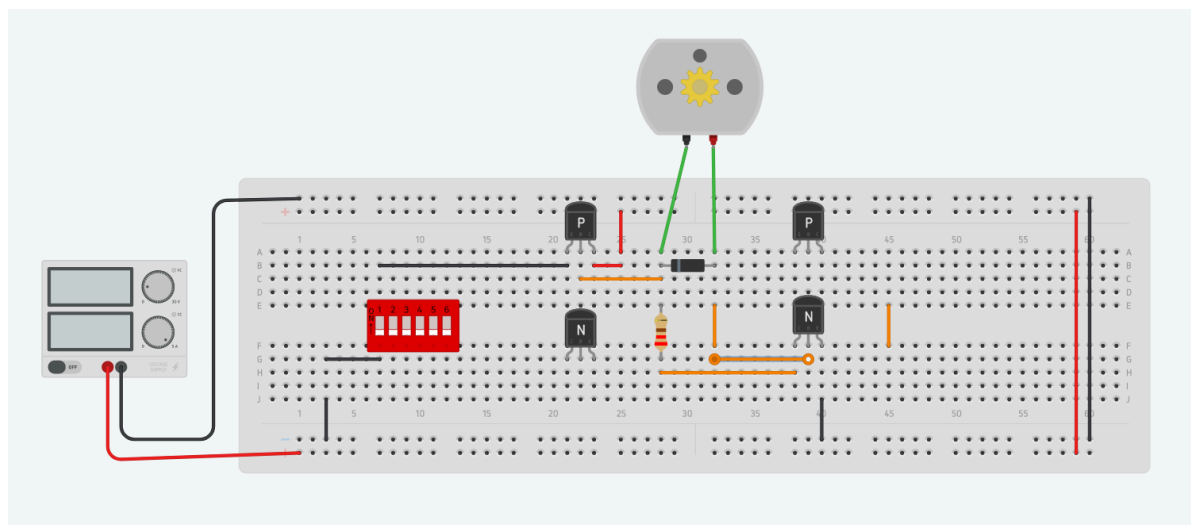We will learn more about DIODES in PART 2



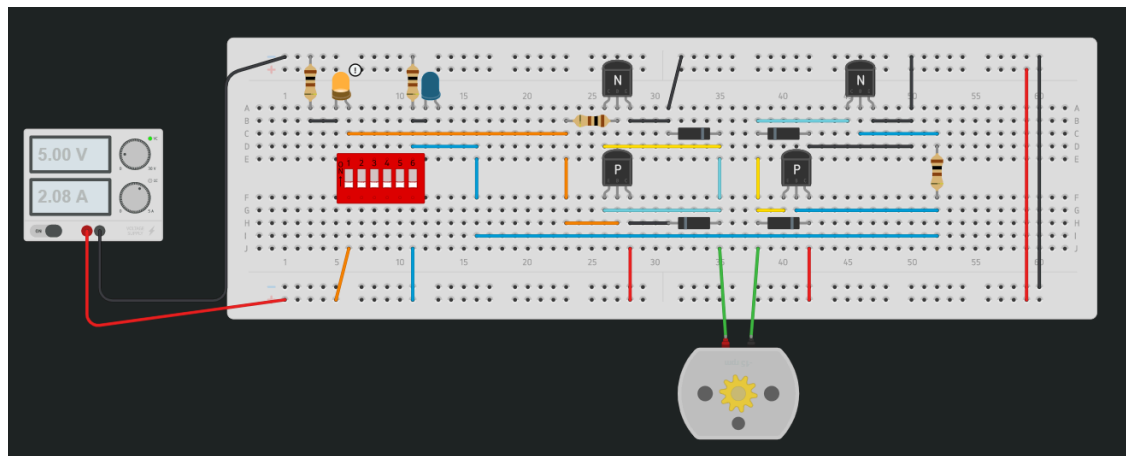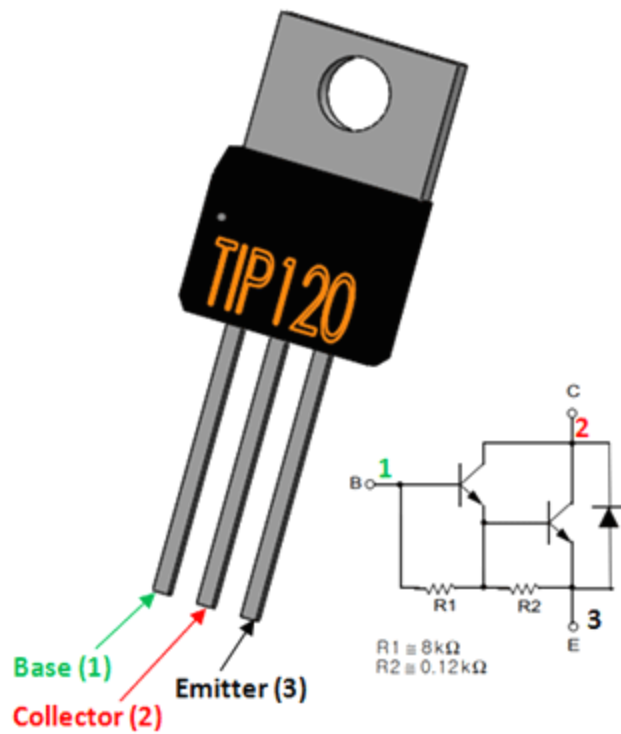

More References

<https://www.build-electronic-circuits.com/h-bridge/>

<https://en.wikipedia.org/wiki/H-bridge>

<https://www.microtype.io/h-bridge-circuit-design/>

<https://electronics.stackexchange.com/questions/386798/why-dont-flyback-diodes-in-h-bridge-damage-power-supply>

Y

<https://forum.arduino.cc/index.php?topic=50931.0>

<https://forum.arduino.cc/index.php?topic=205317.0>

<https://forum.arduino.cc/index.php?topic=590911.0>

<https://forum.arduino.cc/index.php?topic=481875.0>

<https://forum.arduino.cc/index.php?topic=570252.0>

<https://woodgears.ca/motors/dc.html>

<https://www.google.com/url?sa=i&url=https%3A%2F%2Fwww.electricaltechnology.org%2F2020%2F06%2Fdifference-between-ac-dc-motor.html&psig=AOvVaw0b5D5fj50FdhPma06w4dF3&ust=1611069890475000&source=images&cd=vfe&ved=2ahUKEwi8tMGV5aXuAhUtqnIEHZbxBuAQjB16BAgAEAg>

<https://circuitdigest.com/microcontroller-projects/dc-motor-speed-control-using-arduino-and-potentiometer>